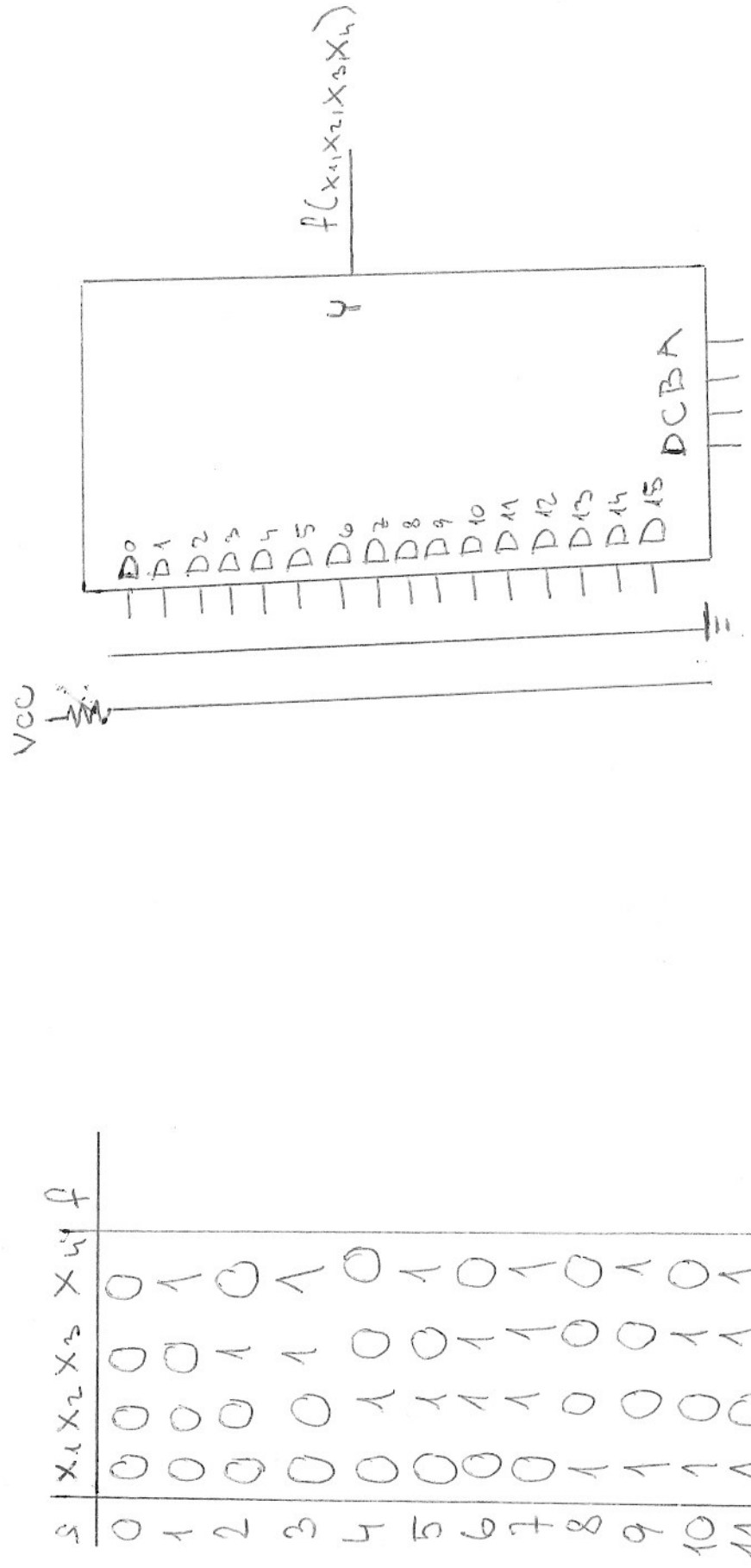


6.3 Pomoci multiplexoru realizujte funkci


$$f(x_1, x_2, x_3, x_4) = \sum(0, 1, 2, 3, 4, 9, 13, 14, 15)$$



6.3 Pomoci multiplexoru realizujte funkci

$$f(x_1, x_2, x_3, x_4) = \sum(0, 1, 2, 3, 4, 9, 13, 14, 15)$$

s	x_1	x_2	x_3	x_4	f
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

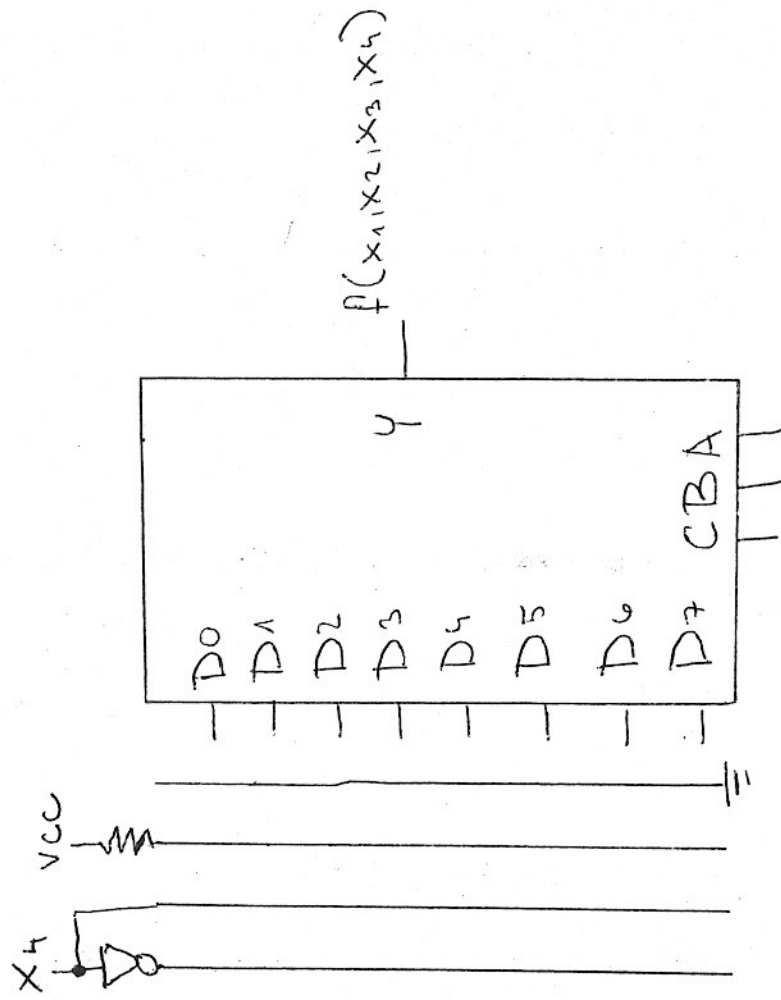


PF. 1

Logickou funkci čtyř
5, 13, 14, 15) realizujte

proměnných $f(x_1, x_2, x_3, x_4) = \sum(0, 1, 2, 3, 4, 5, 13, 14, 15)$
pomocí dekodérů 4-16 a bradla OR.

i	x_4	x_3	x_2	x_1	f
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

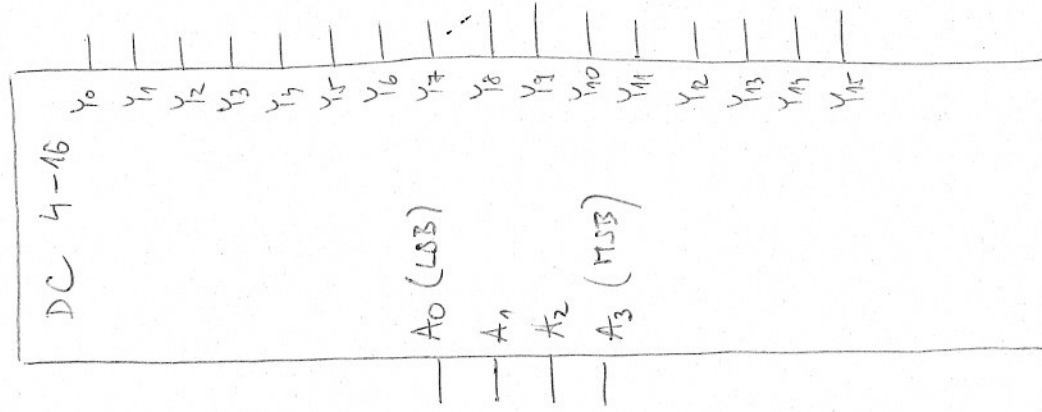


Příklad 6.7)

$$f(a,b,c) = \bar{a} \cdot \bar{b} + abc$$

$$g(a,b,c) = \bar{a} \cdot \bar{b} \bar{c} + ab + bc$$

$$h(a,b,c) = c + \bar{a} \bar{b}$$


PLA

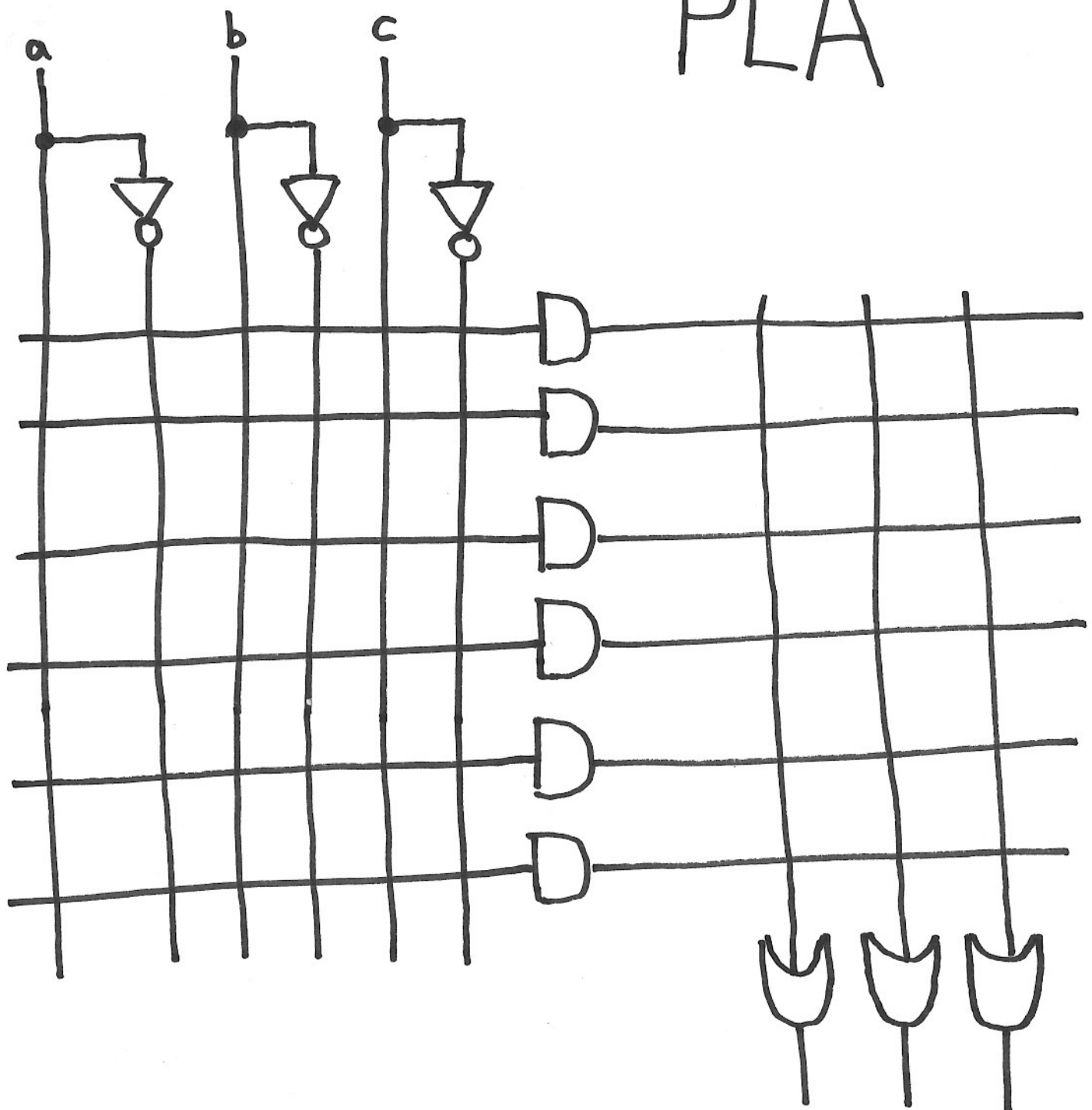

7.24 (dokončení) Realizujte navrženou řídicí jednotku automaticky na obcerstvení pomocí obvodu PLA a RS KO.

	Souč. stav		Vstup		Násl. stav		Výstup				
	Q_1	Q_0	D	N	Q_1^*	Q_0^*		S_1	R_1	S_0	R_0
0φ	0	0	0	0	0	0	0	0	X	0	X
	0	0	0	1	0	1	0	0	X	1	0
	0	0	1	0	1	0	0	1	0	0	X
	0	0	1	1	X	X	X	X	X	X	X
5φ	0	1	0	0	0	1	0	0	X	X	0
	0	1	0	1	1	0	0	1	0	0	1
	0	1	1	0	1	1	1	1	0	X	0
	0	1	1	1	X	X	X	X	X	X	X
10φ	1	0	0	0	1	0	0	X	0	0	X
	1	0	0	1	1	1	1	X	0	1	0
	1	0	1	0	1	1	1	X	0	1	0
	1	0	1	1	X	X	X	X	X	X	X
15φ	1	1	0	0	0	0	0	0	1	0	1
	1	1	0	1	0	1	0	0	1	X	0
	1	1	1	0	1	0	0	X	0	0	1
	1	1	1	1	X	X	X	X	X	X	X

Realizace pomocí PLA a RS KO

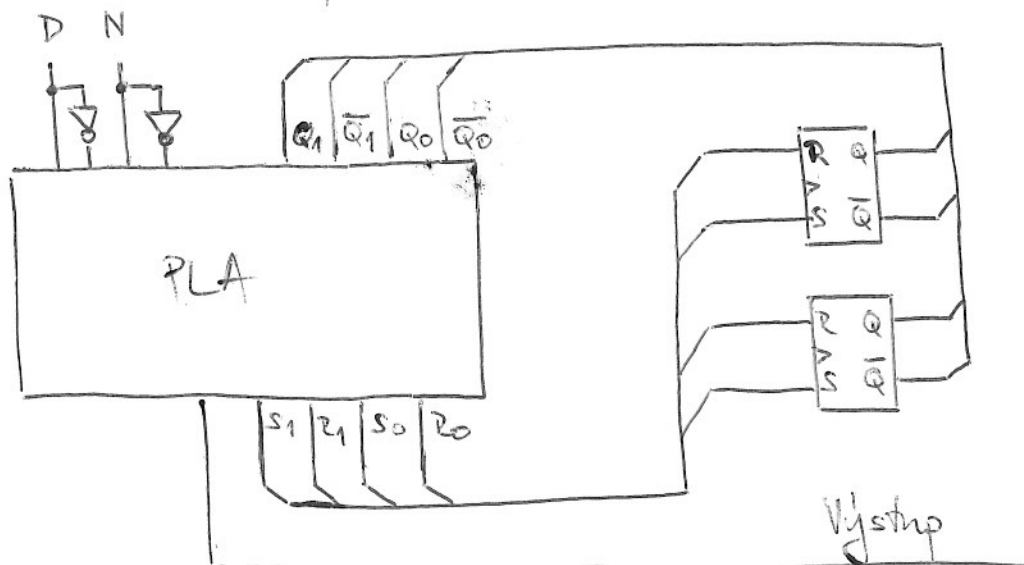

S_0

$Q_1 Q_0 \backslash DN$	00	01	11	10
00	0	1	X	0
01	X	0	X	X
11	0	X	X	0
10	0	1	X	1

R_0

$Q_1 Q_0 \backslash DN$	00	01	11	10
00	X	0	X	X
01	0	1	X	0
11	X	0	X	1
10	X	0	X	0

S_1

$Q_1 Q_0 \backslash DN$	00	01	11	10
00	0	0	X	1
01	0	1	X	1
11	0	0	X	X
10	X	X	X	X

R_1

$Q_1 Q_0 \backslash DN$	00	01	11	10
00	X	X	X	0
01	X	0	X	0
11	1	1	X	0
10	0	0	X	0

V_{setup}

$Q_1 Q_0 \backslash DN$	00	01	11	10
00	0	0	X	0
01	0	0	X	1
11	0	0	X	0
10	0	1	X	1

PLA implementace

