


Příklady popisu obvodů ve VHDL

2025

Vojtěch Mrázek
mrazek@fit.vutbr.cz



Úplná sčítačka (dataflow popis)

 

```
entity FullAdder is  
  port(X, Y, Cin: in bit;    --Inputs  
        Cout, Sum: out bit); --Outputs  
end FullAdder;
```


architecture dataflow of FullAdder is
begin

```
Sum  <= X xor Y xor Cin after 1 ns;  
Cout <= '1' when (X and Y) or (X and Cin) or (Y and Cin) else  
        '0' after 1 ns;
```

end architecture;

- využíváme pouze konstrukce přiřazení signálů
- lze uvést podmínku (when) – vhodné pro popis multiplexoru, dekodéru, ... případně přiřadit zpoždění (after) – pro potřeby simulace

4-bitová sčítačka (strukturní popis)

 

```
entity Adder4 is
  port(
    A, B: in std_logic_vector(3 downto 0);
    Ci: in std_logic;
    S: out std_logic_vector(3 downto 0);
    Co: out std_logic);
end Adder4;
```

architecture structure of Adder4 is

`component FullAdder`

`port(X, Y, Cin: in std_logic; Cout, Sum: out std_logic);`

`end component;`

`signal C: std_logic_vector(3 downto 1);`

`begin`

`FA0: FullAdder port map(A(0),B(0),Ci,C(1),S(0));`

`FA1: FullAdder port map(A(1),B(1),C(1),C(2),S(1));`


`FA2: FullAdder port map(A(2),B(2),C(2),C(3),S(2));`

`FA3: FullAdder port map(X <= A(3),Y <= B(3),
 Cin <= C(3),
 Sum <= S(3), Cout <= Co);`

`end structure;`

- využití konstrukce **component** a **port map** (poziční ne/závislost)
- analogie konstrukce číslicových systémů ze součástek – propojování komponent (součástek) signály (dráty)
- komponenta jako blackbox – pracovat může více vývojářů současně

4-bitová sčítačka (behaviorální popis)

 

```
entity Adder4 is
  port(
    A, B: in std_logic_vector(3 downto 0);
    Ci: in std_logic;
    S: out std_logic_vector(3 downto 0);
    Co: out std_logic);
end Adder4;
```

```
architecture behavioral of Adder4 is
begin
  process (A,B,Ci)
    variable t: std_logic_vector
      (4 downto 0);
  begin
    t := ('0'&A) + ('0'&B) + Ci;
    S <= t(3 downto 0);
    Co <= t(4);
  end process;
end behavioral;
```

```
use IEEE.std_logic_unsigned.all;
```

- využití procesů
- pozor na sensitivity list
(v případě kombinační funkce musí být uveden seznam všech signálů ze kterých je odvozen výsledek)


Implementace základních konstrukcí v SW a HW

sekvence (posloupnost operací)

Sekvence příkazů

```
A = B + C  
D = sin(A)  
Y = F(D)
```

(3 kroky)

 

Implementace základních konstrukcí v SW a HW

selekce (větvení výpočtu)

Podmíněné vykonávání


```
If (S == 0):  
    Y = F(X)  
else:  
    Y = G(X)
```

(3~4 instrukce CPU)

vs.

```
Y = G(X)  
If (S == 0):  
    Y = F(X)
```

(3~5 instrukce CPU)

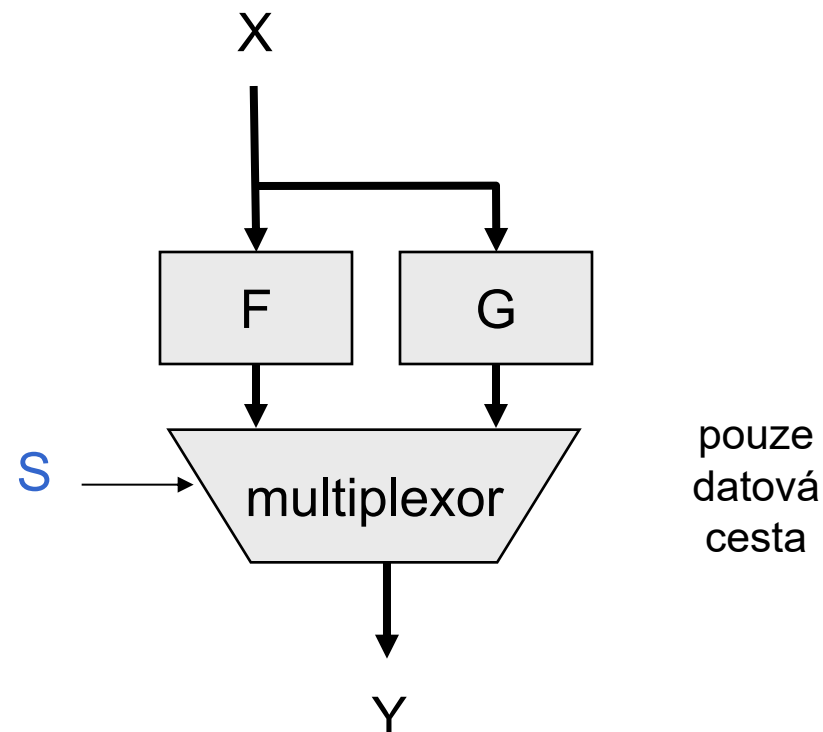


Implementace základních konstrukcí v SW a HW

iterace (opakování výpočtu)

Iterativní zpracování (smyčky)


```
sum = 0
i = 0
while (i < 8):
    sum = sum + mem[i]
    i += 1
```

(cca 40 instrukcí CPU)

 

Obvod realizující iterační součet posloupnosti

- Čítač (Cnt) generuje adresy celého rozsahu paměti (Mem), zastaví se u adresy 7
- Hodnoty (val) z paměti jsou sčítány sčítačkou (Add) a mezivýsledek uchován v registru (Reg)
- Signál EN, zabraňující přepsání finálního výsledku v Reg, je deaktivován po vygenerování nejvyšší adresy paměti
- Signál RST v log. 1 způsobí nulování registru a čítače
- CLK synchronizuje činnost sekvenčních obvodů – čítače a registru
- Po kompletním průchodu pamětí obsahuje Reg (a jeho výstup – signál SUM) součet všech jejích hodnot a signál DONE je aktivní (v log. 0)

 


Návrh obvodu realizujícího iterační součet posloupnosti

- Cílem je navrhnout primitivní obvod, který je schopen vypočítat součet hodnot N (např. 8) prvků umístěných v paměti.
- Praktické použití (po rozšíření): kontrola a generování CRC součtu

```
const N = 8
char mem[N] = {1,...};
char i
char sum;

 sum = 0
for (i=0;i<N;i++)
    sum =  $\oplus$ (sum, mem[i])
```



- Jak převedeme pseudo kód na HW implementaci?
Stačí umět převést sekvenci, selekci, iteraci.

Příklad na papír

Sekvenční sčítačka s využitím komponent

(strukturní popis)

```
entity Acc is
port (
    CLK: in std_logic;
    RST: in std_logic;
    SUM: out std_logic_vector(7 downto 0);
    DONE: out std_logic
);
end Acc;

architecture struct of Acc is

    component Add is
    port (
        A: in std_logic_vector(7 downto 0);
        B: in std_logic_vector(7 downto 0);
        RES: out std_logic_vector(7 downto 0)
    );
    end component;

    component Cnt is
    port (
        CLK: in std_logic;
        RST: in std_logic;
        ADDR: out std_logic_vector(2 downto 0);
        STOP: out std_logic
    );
    end component;

    component Mem is
    port (
        ADDR: in std_logic_vector(2 downto 0);
        VAL: out std_logic_vector(7 downto 0)
    );
    end component;
```

```
component Reg is
port (
    CLK: in std_logic;
    RST: in std_logic;
    EN: in std_logic;
    DIN: in std_logic_vector(7 downto 0);
    DOUT: out std_logic_vector(7 downto 0)
);
end component;


signal addr: std_logic_vector(2 downto 0);
signal val: std_logic_vector(7 downto 0);
signal add_out: std_logic_vector(7 downto 0);
signal reg_out: std_logic_vector(7 downto 0);
signal en: std_logic;

begin

    add_inst: Add port map(A => val, B => reg_out, RES => add_out);
    mem_inst: Mem port map(ADDR => addr, VAL => val);
    cnt_inst: Cnt port map(CLK, RST, addr, en);
    reg_inst: Reg port map(CLK, RST, en, add_out, reg_out);

    SUM <= reg_out;
    DONE <= en;

end struct;
```

 


Model sčítačky (komponenta Add)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity Add is
port (
  A: in std_logic_vector(7 downto 0);
  B: in std_logic_vector(7 downto 0);
  RES: out std_logic_vector(7 downto 0)
);
end Add;

 architecture behav_add of Add is
begin
  RES <= A + B;
end behav_add;
```




Model čítače (komponenta Cnt)

```
entity Cnt is
port (
  CLK: in std_logic;
  RST: in std_logic;
  ADDR: out std_logic_vector(2 downto 0);
  EN: out std_logic
);
end Cnt;

architecture behav of Cnt is
  signal cnt: std_logic_vector(2 downto 0);
begin
  cnt_proc: process(CLK, RST)
  begin
    if RST = '1' then
      cnt <= "000";
      EN <= '1';
    elsif CLK'event and CLK = '1' then
      if cnt = "111" then
        EN <= '0';
      else
        cnt <= cnt + 1;
      end if;
    end if;
  end process;


  ADDR <= cnt;
end behav;
```

 

Model ROM paměti (komponenta Mem)

```
entity Mem is
port (
  ADDR: in std_logic_vector(2 downto 0);
  VAL: out std_logic_vector(7 downto 0)
);
end Mem;


architecture behav_mem of Mem is
begin
  mem: process (ADDR)
  begin
    case ADDR is
      when "000" => VAL <= "00000001";
      when "001" => VAL <= "00000010";
      when "010" => VAL <= "00000011";
      when "011" => VAL <= "00000111";
      when "100" => VAL <= "00001111";
      when "101" => VAL <= "00011111";
      when "110" => VAL <= "00111111";
      when "111" => VAL <= "01111111";
      when others => VAL <= "00000000";
    end case;
  end process;
end behav_mem;
```

 

Model registru (komponenta Reg)

```
entity Reg is
port (
  CLK: in std_logic;
  RST: in std_logic;
  EN: in std_logic;
  DIN: in std_logic_vector(7 downto 0);
  DOUT: out std_logic_vector(7 downto 0)
);
end Reg;

 architecture behav of Reg is
begin
  reg: process (CLK, RST)
  begin
    if RST = '1' then
      DOUT <= "00000000";
    elsif CLK'event and CLK = '1' then
      if EN='1' then
        DOUT <= DIN;
      end if;
    end if;
  end process;
end behav;
```




Model registru (komponenta Reg)

 Příklad využití generických proměnných

```
entity Reg is
generic (
    DATA_WIDTH : integer := 8
)
port (
    CLK: in std_logic;
    RST: in std_logic;
    EN: in std_logic;
    DIN: in std_logic_vector(DATA_WIDTH-1 downto 0);
    DOUT: out std_logic_vector(DATA_WIDTH-1 downto 0)
);
end Reg;

architecture behav of Reg is
begin
    reg: process (CLK, RST)
    begin
        if RST = '1' then
            DOUT <= (others => '0');
        elsif CLK'event and CLK = '1' then
            if EN='1' then
                DOUT <= DIN;
            end if;
        end if;
    end process;
end behav;
```



Sekvenční sčítačka popsaná behaviorálně

```
entity Acc is
port (
    CLK: in std_logic;
    RST: in std_logic;
    SUM: out std_logic_vector(7 downto 0);
    DONE: out std_logic
);
end Acc;

architecture behav of Acc is

    signal addr: std_logic_vector(2 downto 0);
    signal val: std_logic_vector(7 downto 0);
    signal add_out: std_logic_vector(7 downto 0);
    signal reg_out: std_logic_vector(7 downto 0);
    signal stop: std_logic;

begin
    cnt: process (CLK, RST)
    begin
        if RST = '1' then
            addr <= "000";
            stop <= '0';
        elsif clk'event and clk = '1' then
            if addr = "111" then
                stop <= '1';
            else
                addr <= addr + 1;
                stop <= '0';
            end if;
        end if;
    end process;

    with addr select
        val <= "00000001" when "000",
               "00000010" when "001",
               "00000011" when "010",
               "00000111" when "011",
               "00001111" when "100",
               "00011111" when "101",
               "00111111" when "110",
               "01111111" when "111",
               "00000000" when others;

    add_out <= reg_out + val;

    SUM <= reg_out;
    DONE <= not stop;

end behav;
```


```
reg: process (CLK, RST)
begin
    if RST = '1' then
        reg_out <= X"00";
    elsif clk'event and
        clk = '1'
    then
        if stop = '0' then
            reg_out <= add_out;
        end if;
    end if;
end process;

with addr select
    val <= "00000001" when "000",
           "00000010" when "001",
           "00000011" when "010",
           "00000111" when "011",
           "00001111" when "100",
           "00011111" when "101",
           "00111111" when "110",
           "01111111" when "111",
           "00000000" when others;

    add_out <= reg_out + val;

    SUM <= reg_out;
    DONE <= not stop;


end behav;
```

 

Připomenutí principů modelování konečných automatů ve VHDL


Typy konečných automatů

 - Obvod mající paměť lze chápat jako konečný stavový automat (FSM)
- Návrh automatu vyžaduje
 - definovat stavy automatu, přechody mezi stavy a výstupní funkci
- Podle způsobu realizace výstupu rozlišujeme dva základní FSM
 - **Moore** (výstup je pouze funkcí stavu),
 - Mealy (výstup je funkcí stavu a vstupů)



Typy konečných automatů

 - Obvod mající paměť lze chápat jako konečný stavový automat (FSM)
- Návrh automatu vyžaduje
 - definovat stavy automatu, přechody mezi stavy a výstupní funkci
- Podle způsobu realizace výstupu rozlišujeme dva základní FSM
 - Moore (výstup je pouze funkcí stavu),
 - **Mealy** (výstup je funkcí stavu a vstupů)




Implementace konečných automatů ve VHDL

Příklad: detektor posloupnosti 10


- VHDL implementace konečných automatů
 - FSM lze ve VHDL popsat pomocí dvou nebo tří procesů
- Příklad FSM: detektor posloupnosti 10 v řetězci
 - výstupem je 1 pokud byla detekována posloupnost 10

příklad vstupu: 01001110111101010011011

 

odpovídající výstup: 00100001000010101000100

Detektor – Moore FSM – 2 procesy

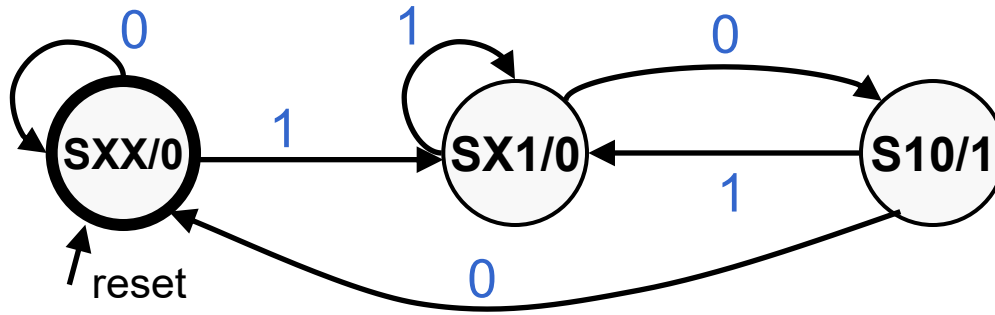

Deklarace signálů

```
type FSMstate is (SXX, SX1, S10);
signal pstate : FSMstate;
signal nstate : FSMstate;
```

```
--Present State register
pstatereg: process(RST, CLK)
begin
    if (RST='1') then
        pstate <= SXX;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Next State logic + output logic
nstate_logic: process(pstate, A)
begin
    nstate <= SXX;
    Y <= '0';
    case pstate is
        when SXX =>
            if (A = '1') then
                nstate <= SX1;
            end if;
        when SX1 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= S10;
            end if;
        when S10 =>
            nstate <= SX1;
            Y <= '1';
            if (A = '0') then
                nstate <= SXX;
            end if;
        when others => null;
    end case;
end process;
```


Detektor – Moore FSM – 3 procesy

```
--Present State register
pstatereg: process (RST, CLK)
begin
    if (RST='1') then
        pstate <= SXX;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Output logic
output_logic: process (pstate)
begin
    Y <= '0';
    case pstate is
        when S10 =>
            Y <= '1';
        when others => null;
    end case;
end process;
```

```
--Next State logic
nstate_logic: process (pstate, A)
begin
    nstate <= SXX;
    case pstate is
        when SXX =>
            if (A = '1') then
                nstate <= SX1;
            end if;
        when SX1 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= S10;
            end if;
        when S10 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= SXX;
            end if;
        when others => null;
    end case;
end process;
```

Detektor – Mealy FSM – 2 procesy

 

Deklarace signálů

```
type FSMstate is (S0, S1);  
signal pstate : FSMstate;  
signal nstate : FSMstate;
```

```
--Present State register  
pstatereg: process(RST, CLK)  
begin  
    if (RST='1') then  
        pstate <= S0;  
    elsif (CLK'event) and (CLK='1') then  
        pstate <= nstate;  
    end if;  
end process;
```

```
--Next State logic + output logic  
nstate_logic: process(pstate, A)  
begin  
    nstate <= S0;  
    Y <= '0';  
    case pstate is  
        when S0 =>  
            if (A = '1') then  
                nstate <= S1;  
            end if;  
        when S1 =>  
            nstate <= S1;  
            if (A = '0') then  
                Y <= '1';  
                nstate <= S0;  
            end if;  
        when others => null;  
    end case;  
end process;
```

Detektor – Mealy FSM – 3 procesy

```
--Present State register
pstatereg: process (RST, CLK)
begin
    if (RST='1') then
        pstate <= S0;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Output logic
output_logic: process (pstate, A)
begin
    Y <= '0';
    if (pstate = S1) and (A = 0) then
        Y <= '1';
    end if;
end process;
```

```
--Next State logic + output logic

nstate_logic: process (pstate, A)
begin
    nstate <= S0;
    case pstate is
        when S0 =>
            if (A = '1') then
                nstate <= S1;
            end if;
        when S1 =>
            nstate <= S1;
            if (A = '0') then
                nstate <= S0;
            end if;
        when others => null;
    end case;
end process;
```

Pozor na sensitivity list u výstupní logiky

Detektor – Mealy FSM – 3 procesy

```
--Present State register
pstatereg: process (RST, CLK)
begin
    if (RST='1') then
        pstate <= S0;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

Výstupní logika nemusí být nutně popsána pomocí procesu

```
--Output logic
Y <= '1' when (pstate = S1) and (A = 0) else
    '0';
```

```
--Next State logic + output logic

nstate_logic: process (pstate, A)
begin
    nstate <= S0;
    case pstate is
        when S0 =>
            if (A = '1') then
                nstate <= S1;
            end if;
        when S1 =>
            nstate <= S1;
            if (A = '0') then
                nstate <= S0;
            end if;
        when others => null;
    end case;
end process;
```